
PCB Design Knowledge Test N°01/2020

Moscow, 15.12.20

Lector: Alexander A. Istomin

To-do until 21.12.20

- You are required to send a well-presented answer sheet in PDF Format written in LaTeX.
 Answers in Russian (English allowed) to the following mail address: pcb_iu10@mail.ru
 No later than: Monday 21.12.2020, 19:00 MSK (GMT+3)
- 2. There will be an oral part (Defense) of the exam (15min max.) where you'll have to explain some of your answers (22/23/24.12)
- Q1: The FT245RL Microcircuit in the **Cryptuino01**, when connected to the PC, creates a communication port (COMx under Windows, /dev/ttyACMx under Linux).
 - a) Write down at least three values (max 5) you can send to this communication port, that, if read, will reset the ATTINY.
 - b) Write down also two values that will put the ATTINY in a working state again.
- Q2: What are the metric dimensions of a 0201(Imperial) Capacitor?
- Q3: What is the standard pitch (there are rare exceptions) for SOIC Chip Pins
- Q4: Is the electric schema dependent on a footprint of one or several components?
- Q5: What is the function of these passive components?

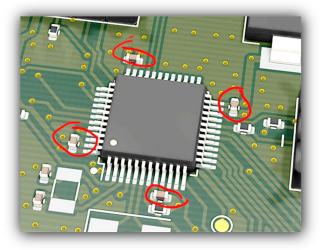

Q6: Can a VIA of 0.6mm/0.3mm exist in a NPTH of 0.4mm?
Q7: What is this symbol?: 1 2°
Q8: What is Edge. Cuts used for?
Q9: Assume the PCB is in the XY Plane. How does the Z-height of a component influence its footprint?
Q10: How (and where) do I indicate in the Schema Editor EESchema) that a component is placed on the backside of the PCB?
Q11: BONUS 1: What is a Rats Nest?
Q12: BONUS 2: What is Eco2. User used for?
Q13: BONUS 3: What does the inscription ORQ on a component or a signal line mean (the line on top)?